

INTRODUCTION TO VLSI DESIGN

November 14, 2020

1 MOSFET Resistance

1.1 Transient Simulation

- Netlist for calculating the R_{eq} as a function of V_{DD} for an NMOS device.

```
1 * C:\Users\SAI ASHOK\hw2_vlsi_q1.cir
  .include "C:\Users\SAI ASHOK\TSMC180.lib"
3 .model nch_tt nmos
  V1 gs 0 DC 1.8
5 M1 ds gs 0 0 nch_tt W=0.24u L=0.18u
  C c1 0 1pF ic=1.8V
7 V2 c1 ds DC 0
  *.IC V(C1)=1.8
9 .control
  let vdd = 1.8V
11 let Req = vector(17)
  let Vval = vector(17)
13 let loop = 0
  print Req[0]
15 while loop<17
    alter @V1=vdd
17    alter @C ic=vdd
    let vdd2 = vdd/2
19    run
    tran 0.05u 500u uic
21    let t_vdd = 0
    let v3 = v(ds)/i(v2)
23    meas tran t_vdd2 when v(ds)=vdd2 cross=1
    meas tran r_eq avg v3 from=t_vdd to=t_vdd2
25    let Req[loop] = r_eq
    let Vval[loop] = vdd
27    let loop=loop+1
    let vdd=vdd-0.1
29 end
  plot req vs vval
31 wrdata plot_1.dat req vs vval
  .endc
33 .end
```

Listing 1: Q1-a.cir

- The value of R_{eq} at $V_{dd} = 1.8V$ is $6.706644e+03\Omega$.

 


Figure 1: nmos

- Please refer Figure 1 for the plot of R_{eq} vs V_{DD} for an NMOS device.
- Netlist for calculating the R_{eq} as a function of V_{DD} for a PMOS device.

```

1 * C:\Users\SAI ASHOK\hw2_vlsi_q1.cir
  .include "C:\Users\SAI ASHOK\TSMC180.lib"
3 .model pch_tt pmos
  V1 gs 0 DC -1.8
5 M1 ds gs 0 0 pch_tt W=0.24u L=0.18u
  C c1 0 1pF ic=-1.8V
7 V2 c1 ds DC 0
  *.IC V(C1)=1.8
9 .control
  let vdd = -1.8V
11 let Req = vector(17)
  let Vval = vector(17)
13 let loop = 0
  print Req[0]
15 while loop<17
    alter @V1=vdd
17    alter @C ic=vdd
    let vdd2 = vdd/2
19    run
    tran 0.05u 500u uic

```

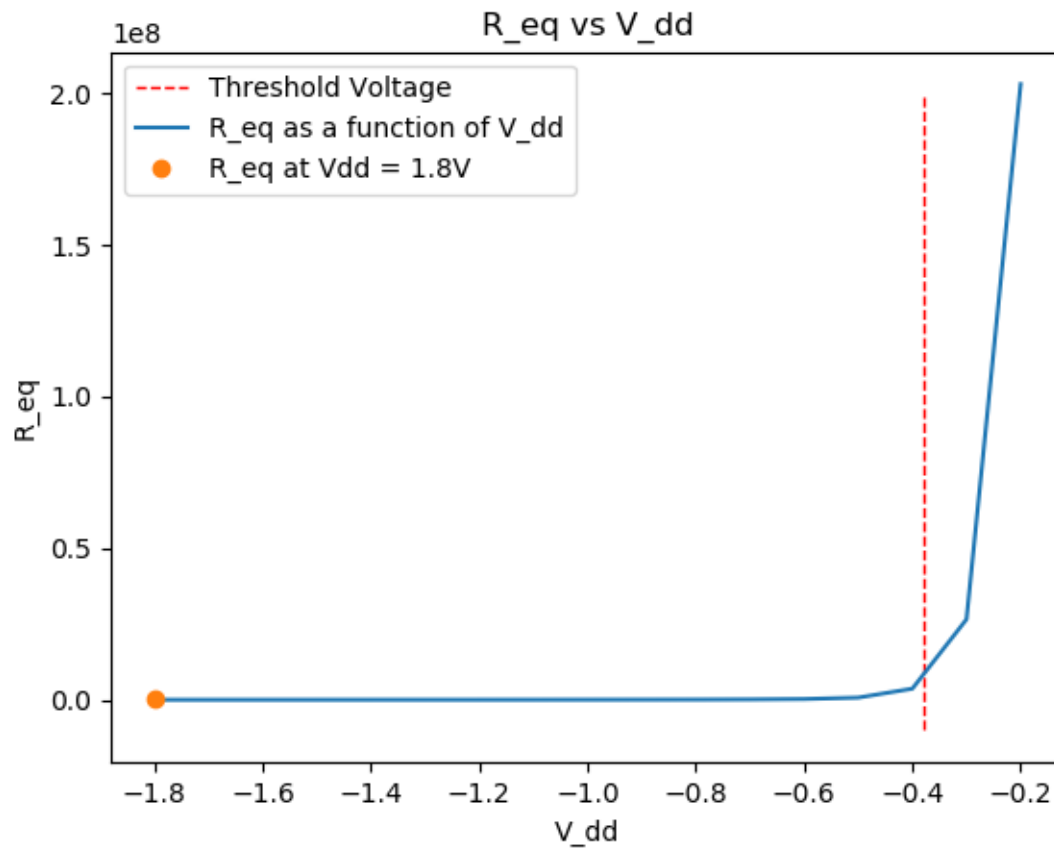


Figure 2: pmos

```

21  let t_vdd = 0
    let v3 = v(ds)/i(v2)
23  meas tran t_vdd2 when v(ds)=vdd2 cross=1
    meas tran r_eq avg v3 from=t_vdd to=t_vdd2
25  let Req[loop] = r_eq
    let Vval[loop] = vdd
27  let loop=loop+1
    let vdd=vdd+0.1
29 end
    plot req vs vval
31 wrdata plot_2.dat req vs vval
    .endc
33 .end

```

Listing 2: Q1-a.cir

- The value of R_{eq} at $V_{dd} = -1.8$ V is 17692Ω .
- Please refer Figure 2 for the plot of R_{eq} vs V_{DD} for a PMOS device.

1.2 Comparing with Table 3.3

- The values of R_{eq} for 0.18 μm process as calculated from simulations are given in the table below.

$ V_{DD} $	R_{eq} NMOS	R_{eq} for PMOS
2V	6477 Ω	15454.38 Ω
1.8V	6706.644 Ω	17692.76 Ω
1.5V	7401.839 Ω	23740.9 Ω
1V	12178.95 Ω	50710.38 Ω
0.5V	275508.9 Ω	726286.9 Ω

- We can clearly observe that these values are less than their counterparts for 0.25 μm process given in the table.
- It is because of the ratio $\frac{\omega}{L}$ which is inversely proportional to R_{eq} .
- It can also be seen from the table that R_{eq} for PMOS devices are much higher than R_{eq} for NMOS devices for the same V_{DD} . This can be attributed to the fact that mobility of holes are less than mobility of electrons.

2 Capacitance

2.1 Long Channel, f=100Hz

- Netlist for simulating capacitance of Long Channel MOS at 100Hz.

```
1 * C:\Users\SAI ASHOK\hw2_vlsi_q2.cir
  .include "C:\Users\SAI ASHOK\TSMC180.lib"
3 .model nch_tt nmos
  V1 N002 0 SINE(0 1.59e-3 10e1)
5 M1 0 N001 0 0 nch_tt W=25u L=10u
  *M1 0 N001 0 0 nch_tt W=0.45u L=0.18u
7 V2 N001 N002 DC -1.8
  .control
9 let Vg = -1.8
  let x = unitvec(72)
11 let y = unitvec(72)
  while Vg < 1.81
13   alter V2=Vg
    tran 1u 1m
15   *tran 1n 100n
    *tran 10p 1n
17   run
    meas tran i_max FIND i(v1) at=0.5m
19   *meas tran i_max MAX i(v1) from=0 to=1n
    let x[20*(Vg+1.8)] = Vg
21   let y[20*(Vg+1.8)] = i_max
    let Vg = Vg + 0.05
23 end
```

 


Figure 3: Long Channel, $f=100\text{Hz}$

```

plot y vs x
25 wrdata plot_3.dat y vs x
   .endc
27 .end

```

Listing 3: Q1-a.cir

- Please refer Figure 3 for the plot.

2.2 Long Channel, $f=10\text{MHz}$

- Netlist for simulating capacitance of Long Channel MOS at 10MHz.

```

1 * C:\Users\SAI ASHOK\hw2_vlsi_q2.cir
  .include "C:\Users\SAI ASHOK\TSMC180.lib"
3 .model nch_tt nmos
  V1 N002 0 SINE(0 1.59e-8 10e6)
5 M1 0 N001 0 0 nch_tt W=25u L=10u
  *M1 0 N001 0 0 nch_tt W=0.45u L=0.18u
7 V2 N001 N002 DC -1.8
  .control
9 let Vg = -1.8
  let x = unitvec(72)

```

 


Figure 4: Long Channel, $f=10\text{MHz}$

```

11 let y = unitvec(72)
   while Vg < 1.81
13   alter V2=Vg
     *tran lu 1m
15   tran ln 100n
     *tran 10p 1n
17   run
     meas tran i_max FIND i(v1) at=50n
19   *meas tran i_max MAX i(v1) from=0 to=1n
     let x[20*(Vg+1.8)] = Vg
21   let y[20*(Vg+1.8)] = i_max
     let Vg = Vg + 0.05
23 end
   plot y vs x
25 wrdata plot_4.dat y vs x
   .endc
27 .end

```

Listing 4: Q1-a.cir

- Please refer Figure 4 for the plot.

2.3 Long Channel, $f=10\text{GHz}$

- Netlist for simulating capacitance of Long Channel MOS at 10GHz.

```
1 * C:\Users\SAI ASHOK\hw2_vlsi_q2.cir
  .include "C:\Users\SAI ASHOK\TSMC180.lib"
3 .model nch_tt nmos
  V1 N002 0 SINE(0 1.59e-11 10e9)
5 M1 0 N001 0 0 nch_tt W=25u L=10u
  *M1 0 N001 0 0 nch_tt W=0.45u L=0.18u
7 V2 N001 N002 DC -1.8
  .control
9 let Vg = -1.8
  let x = unitvec(72)
11 let y = unitvec(72)
  while Vg < 1.81
13   alter V2=Vg
    *tran 1u 1m
15   *tran 1n 100n
    tran 10p 1n
17   run
    *meas tran i_max FIND i(v1) at=50n
19   meas tran i_max MAX i(v1) from=0 to=1n
    let x[20*(Vg+1.8)] = Vg
21   let y[20*(Vg+1.8)] = i_max
    let Vg = Vg + 0.05
23 end
  plot y vs x
25 wrdata plot_5.dat y vs x
  .endc
27 .end
```

Listing 5: Q1-a.cir

- Please refer Figure 5 for the plot.

2.4 Short Channel, $f=100\text{Hz}$

- Netlist for simulating capacitance of Short Channel MOS at 100Hz.

```
* C:\Users\SAI ASHOK\hw2_vlsi_q2.cir
2 .include "C:\Users\SAI ASHOK\TSMC180.lib"
  .model nch_tt nmos
4 V1 N002 0 SINE(0 1.59e-3 10e1)
  *M1 0 N001 0 0 nch_tt W=25u L=10u
6 M1 0 N001 0 0 nch_tt W=0.45u L=0.18u
  V2 N001 N002 DC -1.8
8 .control
  let Vg = -1.8
10 let x = unitvec(72)
  let y = unitvec(72)
12 while Vg < 1.81
```

 


Figure 5: Long Channel, $f=10\text{GHz}$

 


Figure 6: Short Channel, f=100Hz

```

alter V2=Vg
14 tran 1u 1m
   *tran 1n 100n
16 *tran 10p 1n
   run
18 meas tran i_max FIND i(v1) at=0.5m
   *meas tran i_max MAX i(v1) from=0 to=1n
20 let x[20*(Vg+1.8)] = Vg
   let y[20*(Vg+1.8)] = i_max
22 let Vg = Vg + 0.05
end
24 plot y vs x
   wrdata plot_6.dat y vs x
26 .endc
   .end

```

Listing 6: Q1-a.cir

- Please refer Figure 6 for the plot.

2.5 Short Channel, f=10MHz

- Netlist for simulating capacitance of Short Channel MOS at 10MHz.

```

1 * C:\Users\SAI ASHOK\hw2_vlsi_q2.cir
  .include "C:\Users\SAI ASHOK\TSMC180.lib"
3 .model nch_tt nmos
  V1 N002 0 SINE(0 1.59e-8 10e6)
5 *M1 0 N001 0 0 nch_tt W=25u L=10u
  M1 0 N001 0 0 nch_tt W=0.45u L=0.18u
7 V2 N001 N002 DC -1.8
  .control
9 let Vg = -1.8
  let x = unitvec(72)
11 let y = unitvec(72)
  while Vg < 1.81
13   alter V2=Vg
    *tran 1u 1m
15   tran 1n 100n
    *tran 10p 1n
17   run
    meas tran i_max FIND i(v1) at=50n
19   *meas tran i_max MAX i(v1) from=0 to=1n
    let x[20*(Vg+1.8)] = Vg
21   let y[20*(Vg+1.8)] = i_max
    let Vg = Vg + 0.05
23 end
  plot y vs x
25 wrdata plot_7.dat y vs x
  .endc
27 .end

```

Listing 7: Q1-a.cir

- Please refer Figure 7 for the plot.

2.6 Long Channel, $f=10\text{GHz}$

- Netlist for simulating capacitance of Short Channel MOS at 10GHz.

```

1 * C:\Users\SAI ASHOK\hw2_vlsi_q2.cir
  .include "C:\Users\SAI ASHOK\TSMC180.lib"
3 .model nch_tt nmos
  V1 N002 0 SINE(0 1.59e-11 10e9)
5 *M1 0 N001 0 0 nch_tt W=25u L=10u
  M1 0 N001 0 0 nch_tt W=0.45u L=0.18u
7 V2 N001 N002 DC -1.8
  .control
9 let Vg = -1.8
  let x = unitvec(72)
11 let y = unitvec(72)
  while Vg < 1.81
13   alter V2=Vg
    *tran 1u 1m

```

 


Figure 7: Short Channel, $f=10\text{MHz}$

 


Figure 8: Short Channel, $f=10\text{GHz}$

```

15  *tran 1n 100n
    tran 10p 1n
17  run
    *meas tran i_max FIND i(v1) at=50n
19  meas tran i_max MAX i(v1) from=0 to=1n
    let x[20*(Vg+1.8)] = Vg
21  let y[20*(Vg+1.8)] = i_max
    let Vg = Vg + 0.05
23 end
    plot y vs x
25 wrdata plot_8.dat y vs x
    .endc
27 .end

```

Listing 8: Q1-a.cir

- Please refer Figure 8 for the plot.

2.7 Observation

- We can clearly observe that the shape of Graph is not changing in all the cases including short channel, long channel, low frequency and high frequency.

- For the high frequency we can see some distortions because of the sensitivity that lies in calculating for such small step sizes.
- The Peak Capacitance is higher in Long Channel than Short Channel which can be attributed to the fact that $w \cdot L$ of long channel is higher than $W \cdot L$ of short channel as Gate Capacitance is directly proportional to $W \cdot L$.
- Also the Capacitance does not vary for high frequency and low frequency case because of abundance of inversion charges.

3 Simulating NMOS inverter R load

3.1 VTC and Gain of Inverter

- Netlist for simulating Gain and VTC of Inverter.

```

1 * C:\Users\SAI ASHOK\hw2_vlsi_q2.cir
  .include "C:\Users\SAI ASHOK\TSMC180.lib"
3 .model nch_tt nmosV1
  V1 n1 0 2.5
5 R1 n1 Vout 75000
  M1 Vout Vin 0 0 nch_tt W=30u L=10u
7 V2 Vin 0 dc
  .control
9 dc v2 -0.01 2.6 0.01
  run
11 plot vout vs vin
  let gain = deriv(v(vout))
13 let dgain = deriv(gain)
  plot gain vs vin
15 meas dc vil find vin when gain=-1 cross=1
  meas dc vih find vin when gain=-1 cross=2
17 meas dc voh find vout when vin=0 cross=1
  meas dc vol find vout when vin=2.5 cross=1
19 meas dc vm find vout when vin=vout cross=1
  meas dc pg find gain when dgain=0
21 wrdata plot_9.dat vout vs vin
  wrdata plot_10.dat gain vs vin
23 .endc
  .end

```

Listing 9: Q1-a.cir

- Please refer Figure 9 for the plot of VTC.
- Please refer Figure 10 for the plot of Gain.
- Please find the following observations from the simulation.

 


Figure 9: VTC

 


Figure 10: Gain of Inverter

Parameters	Value
V_{IL}	3.871599e-01
V_{IH}	7.738449e-01
V_{OH}	2.499998e+00
V_{OL}	3.174192e-02
V_m	6.731995e-01
$PeakGain$	-9.514598e+01

3.2 Impact of R_L on PeakGain

- Please find the Netlist for simulating Peakgain for various Resistive Loads.

```

* C:\Users\SAI ASHOK\hw2_vlsi_q2.cir
2 .include "C:\Users\SAI ASHOK\TSMC180.lib"
.model nch_tt nmosV1
4 V1 n1 0 2.5
  R1 n1 Vout 75000
6 M1 Vout Vin 0 0 nch_tt W=30u L=10u
  V2 Vin 0 dc
8 .control
  dc v2 -0.01 2.6 0.01 r1 10k 100k 10k
10 run
  plot vout vs vin
12 let gain = deriv(v(vout))
  let dgain = deriv(gain)
14 plot gain vs vin
  wrdata plot_11.dat gain vs vin
16 .endc
.end

```

Listing 10: Q1-a.cir

- Please refer Figure 11 for the plot generated.
- It is clear that as R_L increases Peakgain increases and V_M shifts to the left, which is also supported by the formula in which R_L is directly proportional to Peakgain.
- So as R_L increases the pull down circuit becomes stronger and V_M shifts to the left.

3.3 Transient Analysis for Square Pulse

- Netlist for simulating the output for a square pulse with 50% duty cycle.

```

1 * C:\Users\SAI ASHOK\hw2_vlsi_q5.cir
  .include "C:\Users\SAI ASHOK\TSMC180.lib"
3 .model nch_tt nmos
  V1 n1 0 2.5
5 R1 n1 Vout 75k
  C1 Vout 0 3p
7 M1 Vout Vin 0 0 nch_tt W=0.54u L=0.18u

```

 



Figure 11: Impact of R_L on PG

```

V2 Vin 0 PULSE(0 2.5 0 0 0 2u 4u)
9 .control
tran 0.01u 10u 6u
11 meas tran OP max Vout
    meas tran IP max Vin
13 let va = 0.1*OP
    let vb = 0.9*OP
15 let vc = 0.5*IP
    let vd = 0.5*OP
17 meas TRAN Tr TRIG V(Vout) VAL=va CROSS=1 TARG V(Vout) VAL=vb CROSS=1
    meas TRAN Tf TRIG V(Vout) VAL=vb CROSS=2 TARG V(Vout) VAL=va CROSS=2
19 meas TRAN Tpl TRIG V(Vin) VAL=vc CROSS=1 TARG V(Vout) VAL=vd CROSS=1
    meas TRAN Tph TRIG V(Vin) VAL=vc CROSS=2 TARG V(Vout) VAL=vd CROSS=2
21 .endc
    .end

```

Listing 11: Q1-a.cir

- Please find the following observations from the simulations.

Parameters	Value
t_r	4.940419e-07
t_f	1.437981e-08
t_{plh}	1.543478e-07
t_{phl}	7.799387e-09
t_{pd}	8.107350e-08

- As the charging and discharging path of capacitor are different(because R_L is much higher than effective linearized on-resistance of MOSFET) we have different Rise and Fall times for V_{out} .
- **Geometric Parameters:** Calculating maximum operating frequency depends on t_p , which in turn depends on t_{phl} and t_{plh} . Calculating t_{phl} depends on R_{eq} of MOSFET. For calculating R_{eq} we need I_{dsat} which also depends on W and L of MOSFET which are geometric parameters.
- **Maximum Operating Frequency:** It depends on propagation delay and from the simulated value of propagation delay, we get maximum frequency to be

$$f_{max} = 1/t_p \quad (1)$$

$$f_{max} = 1/81.07ns \quad (2)$$

$$f_{max} = 12.33MHz \quad (3)$$

- **Dynamic Power Dissipation:** It is given by the formulae

$$P_{dyn} = C_L * \Delta V * V_{DD} * f_{max} \quad (4)$$

$$P_{dyn} = 3 * 10^{-12} * (2.5 - 0.463) * 2.5 * 12.33 * 10^6 \quad (5)$$

$$P_{dyn} = 0.225mW \quad (6)$$

3) $V_{DD} = 1.2V$, $V_{TP} = V_{TN} = 0.3V$, C_L initially discharged.

a) Static power when $V_{IN} = 1.2V$? ✓ ✓ ✓ X

→ CMOS inverter does not have a path for current to flow as PMOS is OFF. For the remaining ckt, as all the MOS devices are ON, there is a path for current to flow (so they consume static power)

b) Static power when $V_{IN} = 0V$? X X X X

→ None of Inverters consume static power as the MOSFET whose $V_{in} = V_{in}$ is OFF.

c) V_{OH} of which circuits is $1.2V$? ✓ X ✓ ✓

i) → As the MOS is open $V_{out} = 1.2V$

ii) → As there is no current because of MOSFET whose $V_{in} = V_{in}$, V_{GT} of upper MOSFET should be zero. $V_{out} = 0.9V$.

iii) → As there is no current because below MOSFET is open, upper MOSFET should have $V_{GT} = 0$, $V_{out} = 1.2V$

iv) → As the lower MOS is open, $V_{out} = 1.2V$.

d) Vol of which circuits is 0V? X X X ✓

First three circuits are closed & hence V_{out} cannot be zero.

But the CMOS circuit is open, because of PMOS. $\therefore V_{out} = 0V$.

e) (-) All the circuits except the CMOS circuit are dependent on relative sizes of transistors. ✓ ✓ ✓ X

4) NMOS Inverter

a) * $V_{OH} \rightarrow$ When $V_{in} = 0V$.



No current in circuit

$$V_{OH} = 2.5V$$

~~b)~~ * $V_{OL} \rightarrow$ when $V_{in} = 2.5V$ (NMOS in Linear Region)

$$\frac{k'_n W}{L} \left((V_{DS} - V_T) V_{OL} - \frac{V_{OL}^2}{2} \right) = \frac{V_{DD} - V_{OL}}{R_L}$$

$$345 \times 10^{-6} (75000) \left(2.07 V_{OL} - \frac{V_{OL}^2}{2} \right) = \frac{2.5V - V_{OL}}{1}$$

$$25.875 \left(2.07 V_{OL} - \frac{V_{OL}^2}{2} \right) = 2.5 - V_{OL}$$

$$V_{OL} = 46.329mV$$

* $V_m \rightarrow$ when $V_{in} = V_{out}$ (NMOS in Saturation Region)

$$\frac{k'_n W}{2L} (V_m - V_T)^2 = \frac{V_{DD} - V_m}{R_L}$$

$$12.937 (V_m - 0.43)^2 = 2.5 - V_m$$

$$V_m = 0.7932V$$

b) Expressions for V_{IL} , V_{IH}

$$\frac{dv_{out}}{dv_{in}} = -1 \text{ at } V_{IL} \text{ \& } V_{IH}$$

* V_{IL} (Saturation Region)

$$\frac{V_{DD} - V_{out}}{R_L} = \frac{k' \omega}{2L} (V_{in} - V_T)^2$$

$$\frac{-1}{R_L} \frac{dv_{out}}{dv_{in}} = \frac{k' \omega}{2L} (2)(V_{in} - V_T)$$

$$\frac{1}{R_L} = \frac{k' \omega}{L} (V_{in} - V_T)$$

$$V_{in} = V_{IL} = \frac{L}{k' \omega R_L} + V_T$$

$$= \frac{1}{345 \times 10^{-6} \times 75000} + V_T$$

$$V_{IL} = 0.468V$$

* V_{IH} (Linear Region)

$$\frac{V_{DD} - V_{out}}{R_L} = \frac{k' \omega}{L} \left[(V_{in} - V_T) V_{out} - \frac{V_{out}^2}{2} \right] \quad \text{--- (1)}$$

$$\frac{-1}{R_L} \frac{dv_{out}}{dv_{in}} = \frac{k' \omega}{L} \left[(V_{in} - V_T) \frac{dv_{out}}{dv_{in}} + V_{out} - \cancel{2} \frac{V_{out}}{2} \frac{dv_{out}}{dv_{in}} \right]$$

$$\frac{1}{R_L} = \frac{K'W}{L} [V_T - V_{in} + 2V_{out}]$$

$$\frac{L}{R_L K'W} = V_T - V_{in} + 2V_{out}$$

$$V_{in} = V_T + 2V_{out} - \frac{L}{R_L K'W} \quad (2)$$

using (2) in (1)

$$2.5 - V_{out} = \frac{R_L K'W}{L} \left[\left(2V_{out} - \frac{L}{R_L K'W} \right) V_{out} - \frac{V_{out}^2}{2} \right]$$

$\underbrace{\hspace{10em}}_{25.875} \quad \quad \quad \underbrace{\hspace{10em}}_{0.0386}$

$$V_{out} = 0.25378$$

\Downarrow

$$V_{IH} = V_{in} = 2 \times 0.25378 + 0.43 - 0.0378$$

$$\underline{\underline{V_{IH} = 0.89976}}$$

c) peak gain occurs at V_M

($V_{in} = V_{out}$, Saturation Region)

$$\frac{k'W}{2L} (V_M - V_T)^2 = \frac{V_{DD} - V_{out}}{R_L}$$

$$\left(\frac{k'W}{2L} \right) 2(V_M - V_T) = \frac{-1}{R_L} \frac{dV_{out}}{dV_{in}} \Big|_{V_{in}=V_M}$$

$$- \frac{R_L k'W}{L} (V_M - V_T) = \text{peak gain}$$

$$\therefore \text{peak gain} = 25.875(0.7932 - 0.43)$$

$$= 9.38V$$