

INTRODUCTION TO VLSI DESIGN

October 31, 2020

1 Spice Analysis

1.1 DC Operating point

- Netlist for calculating the DC operating point for the given filter.

```
1 * C:\Users\SAI ASHOK\q1_vlsi1.cir
  R1 Vout N001 1000
3 C1 Vout N002 0.000001
  R2 N002 0 100
5 V1 N001 0 2.5
  *control commands
7 .control
  op
9 print v(vout)
  .endc
11 .end
```

Listing 1: Q1-a.cir

- The Simulated value of V_{out} is 2.5V.

1.2 Phase Difference using Transient Analysis

- Phase lag introduced at $f = 100\text{Hz}$ as observed from simulations is -31.3216° .
- Netlist for calculating the phase lag between input and output at $f = 100\text{Hz}$.

```
1 * C:\Users\SAI ASHOK\q1_vlsi2.cir
  R1 Vout Vin 1000
3 C1 Vout N001 0.000001
  R2 N001 0 100
5 V1 Vin 0 SINE(0 1 100)
  *control commands
7 .control
  tran 0.02 20ms
9 meas TRAN TIME_1 TRIG V(Vin) VAL=0 CROSS=2 TARG V(Vin) VAL=0 CROSS=4
  meas TRAN TIME_2 TRIG V(Vin) VAL=0 CROSS=2 TARG V(Vout) VAL=0 CROSS=2
11 print 360*(time_2/time_1)
  *plot vout vin
13 wrdata plot1.dat V(Vout)
  wrdata plot2.dat V(Vin)
15 .endc
  .end
```

 


Figure 1: Phase Difference at $f=100\text{Hz}$

Listing 2: Q1-a.cir

- Please refer Figure-1 for the output generated by SPICE simulator.
- Phase lag introduced at $f = 1\text{MHz}$ as observed from simulations is -0.165° .
- Netlist for calculating the phase lag between input and output at $f = 1\text{MHz}$.

```
* C:\Users\SAI ASHOK\q1_vlsi2.cir
2 R1 Vout Vin 1000
  C1 Vout N001 0.000001
4 R2 N001 0 100
  V1 Vin 0 SINE(0 1 1000000)
6 *control commands
  .control
8 tran 2n 0.000002
  meas TRAN TIME_1 TRIG V(Vin) VAL=0 CROSS=2 TARG V(Vin) VAL=0 CROSS=4
10 meas TRAN TIME_2 TRIG V(Vin) VAL=0 CROSS=2 TARG V(Vout) VAL=0 CROSS=2
  print 360*(time_2/time_1)
12 *plot vout vin
  wrdata plot1.dat V(Vout)
```

 


Figure 2: Phase Difference at $f=1\text{MHz}$

```
14 wrdata plot2.dat V(Vin)
   .endc
16 .end
```

Listing 3: Q1-a.cir

- Please refer Figure-2 for the output generated by SPICE simulator.

1.3 Characteristics of Transfer Function

- Netlist used for simulating Amplitude and Phase characteristics of the given RC circuit.

```
* C:\Users\SAI ASHOK\q1_vlsi3.cir
2 R1 Vout Vin 1000
  C1 Vout N001 0.000001
4 R2 N001 0 100
  V1 Vin 0 dc 0 ac 1
6 .control
  ac dec 10 0.1 1000000
8 run
  *Magnitude of output on log scale
10 wrdata plot1.dat db(vout/vin) xlog
   *plot db(vout/vin) xlog
```

 


Figure 3: Magnitude Response

```

12 *Phase of output on log scale
   wrdata plot2.dat {180/3.14*phase(vout/vin)} xlog
14 *plot {180/3.14*phase(vout/vin)} xlog
   .endc
16 .end

```

Listing 4: Q1-a.cir

- The phase corresponding to -3dB is -40° (approx) as observed from simulations.
- Please refer Figure-3 and Figure-4 for Magnitude and Phase plots of Transfer function.

2 SPICE simulation for diode circuit

2.1 Simulation

- Netlist for simulating the diode taking $I_s = 10^{-14}$.

```

* C:\Users\SAI ASHOK\q2_vlsi1.cir
2 .model DMOD D
  D1 N002 P001 DMOD
4 R1 N001 N002 2000
  V1 N001 0 2.5

```

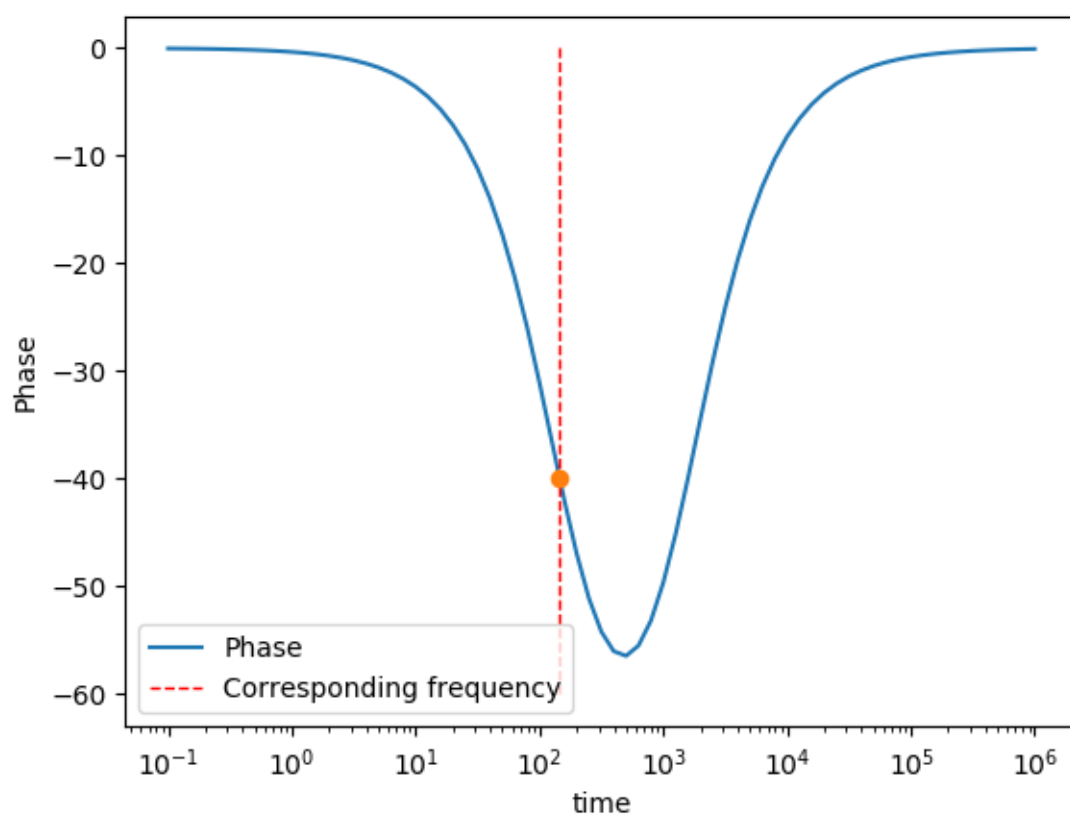


Figure 4: Phase Response

```

6 R2 P001 N003 2000
  D2 N003 0 DMOD
8 .op
  .control
10 run
  *display
12 print i(v1)
  .endc
14 .end

```

Listing 5: Q1-a.cir

- Value of I_d from simulations is $-3.12e-04$ and voltage across diode comes out to be 0.625V.

3 Controlled Sources

- Netlist for simulating the given circuit consisting of a VCCS.

```

* C:\Users\SAI ASHOK\q3_vlsi1.cir
2 G1 0 Vout N001 0 1000000
  R1 Vin N001 1000
4 R2 Vout N001 3000
  V1 0 Vin SINE(0 0.5 1000)
6 R3 Vout 0 1
  .control
8 tran 50u 5m
  run
10 *plot Vout Vin
  wrdata plot1.dat Vout
12 wrdata plot2.dat Vin
  .endc
14 .end

```

Listing 6: Q1-a.cir

- Gain is observed to be -3 from the simulations.
- Please refer Figure-5 for the simulated output.

4 MOSFET characteristics

4.1 I_d vs V_{ds}

- Netlist for simulating a Short Channel nmos.

```

* C:\Users\SAI ASHOK\q4_vlsi1.cir
2 .include "C:\Users\SAI ASHOK\TSMC180.lib"
  .model nch_tt nmos
4

```

 


Figure 5: VCCS

 


Figure 6: Short Channel nmos characteristics

```

1 *M1 ds gs 0 0 nch_tt W=15u L=10u
6 M1 ds gs 0 0 nch_tt W=0.27u L=0.18u
V1 ds 0 DC 0
8 V2 gs 0 DC 1
  .dc V1 0 1.8 0.01
10 .control
  run
12 *plot -i(v1) vs v(ds)
  wrdata plot1.dat -i(v1) vs v(ds)
14 .endc
  .end

```

Listing 7: Q1-a.cir

- Please refer Figure-6 for simulated output.
- Netlist for simulating a Long Channel nmos.

```

1 * C:\Users\SAI ASHOK\q4_vlsi1.cir
  .include "C:\Users\SAI ASHOK\TSMC180.lib"
3 .model nch_tt nmos

5 M1 ds gs 0 0 nch_tt W=15u L=10u
  *M1 ds gs 0 0 nch_tt W=0.27u L=0.18u

```

 



Figure 7: Long Channel nmos characteristics

```

7 V1 ds 0 DC 0
  V2 gs 0 DC 1
9 .dc V1 0 1.8 0.01
  .control
11 run
   *plot -i(v1) vs v(ds)
13 wrdata plot1.dat -i(v1) vs v(ds)
   .endc
15 .end

```

Listing 8: Q1-a.cir

- Please refer Figure-7 for simulated output.
- Netlist for simulating a Short Channel pmos.

```

1 * C:\Users\SAI ASHOK\q4_vlsi1.cir
  .include "C:\Users\SAI ASHOK\TSMC180.lib"
3 .model pch_tt pmos

5 *M1 ds gs 0 0 nch_tt W=15u L=10u
  M1 ds gs 0 0 nch_tt W=0.27u L=0.18u
7 V1 ds 0 DC 0
  V2 gs 0 DC -1

```

 


Figure 8: Short Channel pmos characteristics

```

9 .dc V1 0 -1.8 -0.01
  .control
11 run
  *plot -i(v1) vs v(ds)
13 wrdata plot1.dat -i(v1) vs v(ds)
  .endc
15 .end

```

Listing 9: Q1-a.cir

- Please refer Figure-8 for simulated output.
- Netlist for simulating a Long Channel pmos.

```

1 * C:\Users\SAI ASHOK\q4_vlsi1.cir
  .include "C:\Users\SAI ASHOK\TSMC180.lib"
3 .model pch_tt pmos

5 M1 ds gs 0 0 pch_tt W=15u L=10u
  *M1 ds gs 0 0 pch_tt W=0.27u L=0.18u
7 V1 ds 0 DC 0
  V2 gs 0 DC -1
9 .dc V1 0 -1.8 -0.01
  .control

```

 


Figure 9: Long Channel pmos characteristics

```

11 run
   *plot -i(v1) vs v(ds)
13 wrdata plot1.dat -i(v1) vs v(ds)
   .endc
15 .end

```

Listing 10: Q1-a.cir

- Please refer Figure-9 for simulated output.

4.2 Saturation and Linear Regions

- Saturation and Linear Regions have been identified using I_d vs $V_{gs} - V_{th}$ plot.
- Netlist used for simulating the I_d vs V_{gs} plot for MOS devices. (Please note that the same netlist can be used for nmos short and long channel, pmos short and long channel with minor modifications)

```

1 * C:\Users\SAI ASHOK\q4_vlsi1.cir
  .include "C:\Users\SAI ASHOK\TSMC180.lib"
3 .model pch_tt pmos
5 *M1 ds gs 0 0 pch_tt W=15u L=10u

```

 


Figure 10: Short Channel nmos

```

M1 ds gs 0 0 pch_tt W=0.27u L=0.18u
7 V1 ds 0 DC -1.8
V2 gs 0 DC 0
9 .dc V2 0 -2.5 -0.01
.control
11 run
plot -i(v1) vs v(gs)
13 wrdata plot1.dat -i(v1) vs v(gs)
.endc
15 .end

```

Listing 11: Q1-a.cir

- Please refer Figure-10 for Short channel nmos.
- Please refer Figure-11 for Long Channel nmos.
- Please refer Figure-12 for Short channel pmos.
- Please refer Figure-13 for Long Channel pmos.
- **Please note that the region to the right of I_d vs $V_{gs} - V_{th}$ graph is saturation region and on the left would be Linear Region.**

 


Figure 11: Long Channel nmos

 


Figure 12: Short Channel pmos

 


Figure 13: Long Channel pmos

 


Figure 14: NMOS SC

4.3 Small Signal Resistance

- Small Signal Resistance is 1 over slope of I_d vs V_{ds} curve in saturation region.

MOS device	Slope	Small Signal Resistance
NMOS Short Channel	1.19e-05	84033 Ω
NMOS Long Channel	1.18e-05	84745 Ω
PMOS Short Channel	2.81e-06	355871 Ω
PMOS Long Channel	5.13e-07	1960784 Ω

4.4 Sub Threshold Slope

- Previously generated plots of I_d vs $V_{gs} - V_{th}$ for nmos short channel device in Log-Lin scale. (Please refer Figure-14)
- Slope of Sub-Threshold region = 11.40
- Value of $n = 190$

 


Figure 15: NMOS LC

- Previously generated plots of I_d vs $V_{gs} - V_{th}$ for nmos long channel device in Log-Lin scale. (Please refer Figure-15)
- Slope of Sub-Threshold region = 10.436
- Value of n = 174
- Previously generated plots of I_d vs $V_{gs} - V_{th}$ for pmos short channel device in Log-Lin scale. (Please refer Figure-16)
- Slope of Sub-Threshold region = -10.427
- Value of n = -174
- Previously generated plots of I_d vs $V_{gs} - V_{th}$ for pmos long channel device in Log-Lin scale. (Please refer Figure-17)
- Slope of Sub-Threshold region = -9.994
- Value of n = -166.5

 


Figure 16: PMOS SC

 


Figure 17: PMOS LC

 


Figure 18: Propagation delay

5 Propagation Delay

5.1 Rise time and Propagation delay

- Netlist used to simulate the circuit with step input. Value of $R = 1000\Omega$, $C = 1\mu F$, $RC = 1ms$.

```

1 * C:\Users\SAI ASHOK\q5_vlsi1.cir
  V1 N001 0 PULSE(0 1 0 0 0 5 5 0)
3 R1 Vout N001 1000
  C1 Vout 0 0.000001
5 *control commands
  .control
7 tran 0.1u 40ms
  plot vout
9 .endc
  .end

```

Listing 12: Q1-a.cir

- Please refer Figure-18 for the output of simulation.
- As we can observe from the graph t_p is 0.000649351, which is approximately equal to $0.69RC$ (0.00069).

 


Figure 19: t_p vs $t_{r,in}$

- As we can observe from the graph t_r is $0.00233766 - 0.00012987 = 0.0022077$, which is approximately equal to $2.2RC$ (0.002200).

5.2 Non-Ideal Step Input

- Netlist to simulating for Non-Ideal Step Input and then to calculate Propagation Delay.

```

* C:\Users\SAI ASHOK\q5_vlsi1.cir
2 V1 N001 0 PULSE(0 1 0 0.01n 0 5 5 0)
R1 Vout N001 1000
4 C1 Vout 0 0.000001
*control commands
6 .control
tran 0.1u 1ms
8 meas TRAN TIME_1 TRIG V(Vout) VAL=0 CROSS=1 TARG V(Vout) VAL=0.5 CROSS=1
plot vout
10 .endc
.end


```

Listing 13: Q1-a.cir

- Please refer Figure-19 for the plot Propagation delay vs Rise time of Input

1)

b) phase lag estimation.

 

$$V_{in} - iR - iR_E - V_C = 0$$

$$V_{in} - RC \frac{dV_C}{dt} - R_E \frac{dV_C}{dt} - V_C = 0 \quad \text{Let } R + R_E = R'$$

$$V_{in} = R' C \frac{dV_C}{dt} + V_C \quad (\text{applying Laplace transform})$$

$$V_{in}(s) = V_C(1 + R'Cs)$$

$$V_C = \frac{V_{in}(s)}{1 + R'Cs}$$

$$\text{W.K.T } i = C \frac{dV_C}{dt}$$

$$I(s) = Cs V_C(s)$$

$$I(s) = \frac{Cs V_{in}(s)}{1 + R'Cs}$$

$$V_{out} = I(s)R_L + V_C(s)$$

$$V_{out}(s) = \frac{R_L C s V_{in}(s)}{1 + R_L' C s} + \frac{V_{in}(s)}{1 + R_L' C s}$$

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{1 + R_L C s}{1 + R_L' C s} \quad \left. \vphantom{\frac{V_{out}(s)}{V_{in}(s)}} \right\} \text{transfer function.}$$

$$\text{phase lag introduced} = \underbrace{\tan^{-1}\left(\frac{R_L C \omega}{1}\right)}_{\text{numerator}} - \underbrace{\tan^{-1}\left(\frac{R_L' C \omega}{1}\right)}_{\text{denominator}}$$

$$\begin{aligned} \text{for } f = 100 \text{ Hz} &\Rightarrow \tan^{-1}(100 \times 10^6 \times 2\pi \times 100) - \tan^{-1}(1100 \times 10^6 \times 2\pi \times 100) \\ &= 3.5952^\circ - 34.650^\circ \\ &= -31.055^\circ \end{aligned}$$

$$\begin{aligned} \text{for } f = 1000000 \text{ Hz} &\Rightarrow \tan^{-1}(100 \times 10^6 \times 2\pi \times 10^6) - \tan^{-1}(1100 \times 10^6 \times 2\pi \times 10^6) \\ &= -0.08289^\circ \end{aligned}$$

c) phase lag introduced at 3dB point.

→ in the (b) part we have calculated Transfer function.

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{1 + R_2 C s}{1 + R_1' C s} = \frac{1 + R_2 C \omega j}{1 + R_1' C \omega j}$$

* 3dB point

$$\frac{\sqrt{1 + (R_2 C \omega)^2}}{\sqrt{1 + (R_1' C \omega)^2}} = \frac{1}{\sqrt{2}}$$

$$1 = ((R_1')^2 - 2R_2^2) C^2 \omega^2$$

$$\omega^2 = 840336.134$$

$$\omega_1 = 916.698$$

* corresponding phase lag:


$$\rightarrow \tan^{-1}(R_2 C \omega_1) - \tan^{-1}(R_1' C \omega_1)$$

$$\Rightarrow (-0.6981) \times \frac{1}{\pi} \cdot (180^\circ/\pi) = \underline{\underline{-40.001^\circ}}$$

2)

a) Replacing diode with a voltage source

$$V_{D_{on}} = 0.7V$$

 

Evaluation:

$$0 + 2.5 - i(2000) - 0.7 - i(2000) - 0.7 = 0$$

$$2.5 - 1.4 = i(4000)$$

$$\frac{1.1}{4000} = i$$

$$i = \underline{0.000275}$$

b) Solving for I_D & V_D using Ideal Diode equation


Ideal diode Equation:

$$I_D = I_s (e^{\frac{qV_D}{nKT}} - 1) \quad \text{--- (1)}$$

Loop Equation:

$$2.5 - I_D(4000) - 2V_D = 0$$
 
$$I_D = \frac{2.5 - 2V_D}{4000} \quad \text{--- (2)}$$



using eqn (2) in (1):

$$e^{\frac{V_D}{0.026}} = 1 + \frac{10^4 (2.5 - 2V_D)}{1}$$

$$V_D = 0.638V$$

$$I_D = 0.000306 \text{ Amps.}$$

4)

b) differences between short & long channel MOSFET

- * Long channel transistor ~~nm~~ has saturated dependence of I_D as a function of V_{DS} in the saturation region. (Clearly observable from the spacing between different curves).
- * Short channel MOSFET has a linear dependence of saturation current w.r.t V_{DS} which is also apparent in the graph.
- * Short channel Transistors also saturate at a lower voltage than Long channel transistors (V_{DS}) (in case of nmos)
- * The above stated velocity saturation is less prominent in pmos.